



Home  
Prerequisites  
Syllabus

Course

Book  
Software  
Terms  
Papers  
Talks  
Cool Stuff  
About  
Team  
Q&A

## Project 2: Combinational Chips

### Background

The centerpiece of the computer's architecture is the *CPU*, or *Central Processing Unit*, and the centerpiece of the CPU is the *ALU*, or *Arithmetic-Logic Unit*. In this project you will gradually build a set of chips, culminating in the construction of the *ALU* chip of the *Hack* computer. All the chips built in this project are standard, except for the *ALU* itself, which differs from one computer architecture to another.

### Objective

Build all the chips described in Chapter 2 (see list below), leading up to an *Arithmetic Logic Unit* - the Hack computer's ALU. The only building blocks that you can use are the chips described in chapter 1 and the chips that you will gradually build in this project.

### Chips

Chip (HDL)	Description	Test script	Compare file
<a href="#">HalfAdder</a>	Half Adder	<a href="#">HalfAdder.tst</a>	<a href="#">HalfAdder.cmp</a>
<a href="#">FullAdder</a>	Full Adder	<a href="#">FullAdder.tst</a>	<a href="#">FullAdder.cmp</a>
<a href="#">Add16</a>	16-bit Adder	<a href="#">Add16.tst</a>	<a href="#">Add16.cmp</a>
<a href="#">Inc16</a>	16-bit incrementer	<a href="#">Inc16.tst</a>	<a href="#">Inc16.cmp</a>
<a href="#">ALU</a>	Arithmetic Logic Unit	<a href="#">ALU.tst</a>	<a href="#">ALU.cmp</a>

### Contract

When loaded into the supplied *Hardware Simulator*, your chip design (modified `.hdl` program), tested on the supplied `.tst` script, should produce the outputs listed in the supplied `.cmp` file. If that is not the case, the simulator will let you know.

### Resources

The relevant reading for this project is [Chapter 2](#) and [Appendix A](#). Specifically, all the chips described in Chapter 2 should be implemented in the *Hardware Description Language* (HDL) specified in Appendix A.

For each chip, we supply a skeletal `.hdl` file with a missing implementation part. In addition, for each chip we supply a `.tst` script that instructs the hardware simulator how to test it, and a `.cmp` ("compare file") containing the correct output that this test should generate. Your job is to complete and test the supplied skeletal `.hdl` files.

The resources that you need for this project are the supplied *Hardware Simulator* and the files listed above. If you've downloaded the *Nand2Tstris Software Suite*, these files are stored in your `projects/02` directory.

### Tips

**Use built-in chips:** Your HDL programs will most likely include chip parts that you've built in project 1. As a rule, though, we recommend using the built-in versions of these chips instead. The use of built-in chips ensures correct, efficient, and predictable simulation. There is a simple way to accomplish this convention: make sure that your project directory includes only the `.hdl` files of the chips developed in the current project.

**Implementation order:** We recommend building the chips in the order in which they appear in Chapter 2. However, since the simulator features built-in versions of these chips, you can use chip-parts without first building them: the simulator will automatically use their built-in implementations.